

# Counters

7A

&

7B

- for digital counting.
  - Here, we have Binary numbering system, 0, 1
  - In Binary, ~~the~~ sequence of upcounting & downcounting same.
  - In given ~~eg~~.
- All zeroes advance to all ones in  $2^n$  steps.


01

$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

4 bits.
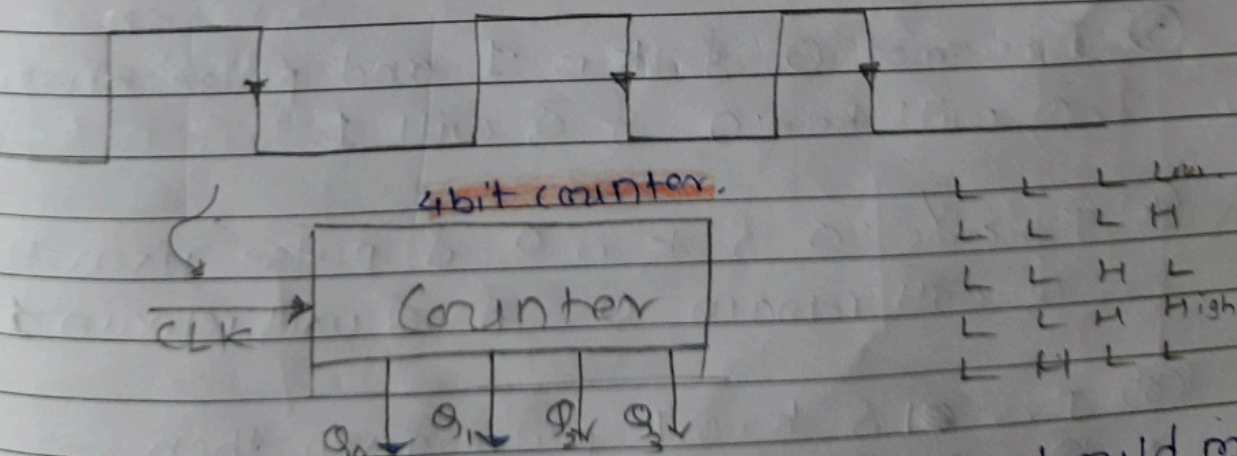
## \* Application.

eg. At industry pens are moving on conveyor belt by using infrared sensors & LED displayed count




When one falling edge comes counter should move to next step.

initially output all is '0' (low) then \*



\* M/slave.

 

CLK	J	K	Q	$\bar{Q}$
0, 1	X	X	LS	
$\uparrow\downarrow$	0	0	LS	
$\uparrow\downarrow$	0	1	0	1
$\uparrow\downarrow$	1	0	1	0
$\uparrow\downarrow$	1	1	Toggle	


- Whatever input at time of rising edge of JK flip-flop are considered master inside that is copied by slave in falling edge.

For M/slave output (0,1) or (1,0) only

- \* For (1,1) input output is Toggle i.e.  $\bar{LS}$  (reverse of LS)  
Perfor exp.

IF

 - ① J is 1 & K is 0 and pulse is given, then Q will 1 &  $\bar{Q}$  will 0



- ② J is <sup>become</sup> 0 & K is 0 and Pulse is given, then Q will remain 1 &  $\bar{Q}$  will remain 0.

Output depends on previous state.


- ③ J become 0 & K is 1 and pulse given, then Q will become 0 &  $\bar{Q}$  will 1

- ④ J become <sup>is</sup> 0 & K is 0 & pulse given then, Q will remain 0 &  $\bar{Q}$  will remain 1

- ⑤ J is 0 & K is 1 pulse given then Q will invert to 1 &  $\bar{Q}$  will invert to 0

 - ⑥ J is 1 & K is 1 pulse given then, Q will invert again to 0 &  $\bar{Q}$  to 1





(Master reset)


is an overriding input over all combination.

It forces flip-flop to go to reset state.

$\overline{MR}$	CLK	J	K	Q	$\overline{Q}$
0	X	X	X	0	1
1	0	X	X	LS	LS
1	1	0	0	LS	LS
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	$\overline{Q}$	Q

Toggle
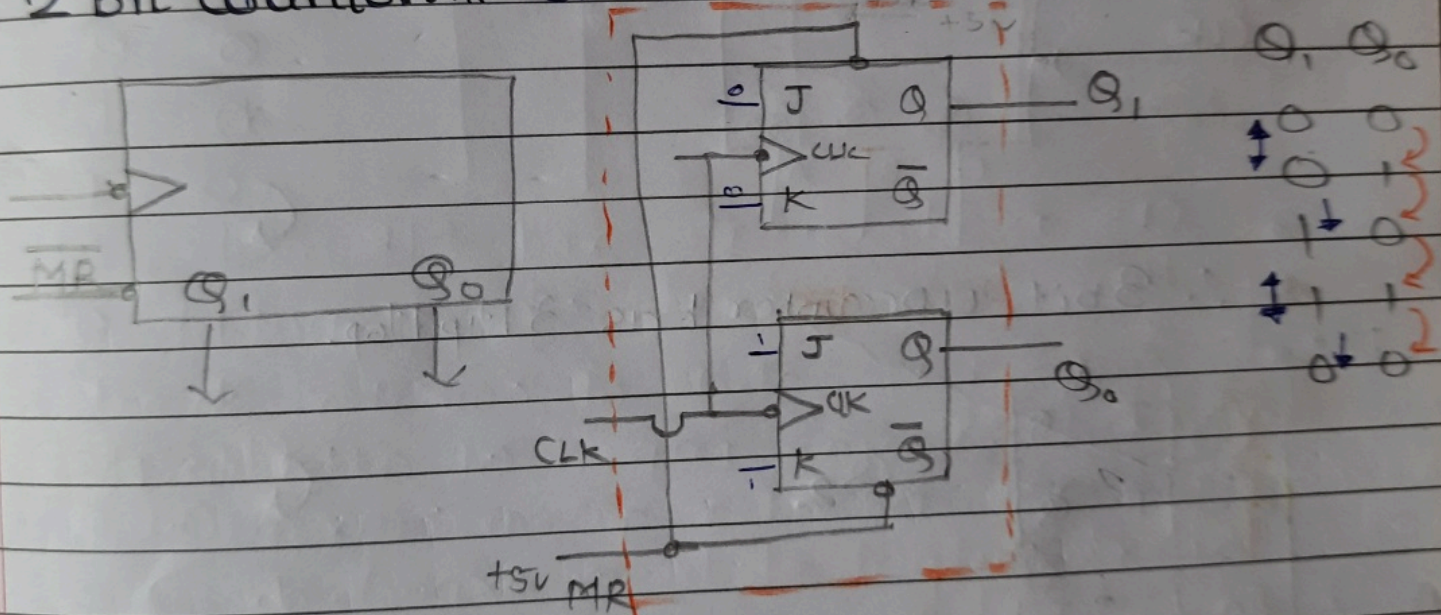
## \* 2 bit Counter.\* [For each bit - 1 Flip-Flop]



After each/every clock output must go on  
Here  $Q_0$  always toggle.


- \* When  $Q_0$  is changes to from 1 to 0.
- \* When  $Q_0$  is 0 then next state of  $Q_1$  is continuous & if  $Q_0$  is 1 then next state of  $Q_1$  is toggle.

Input J, K, (0, 0) if want to conti.  
(1, 1) ——— toggle.



# Design of Counters.

eg 4 bit counter.

 


$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

\* In General.


n-bit Binary upcounter **UP-COUNTER**

\* consider 3 bit counter

 

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


∴ 3 bit upcounter has 3 flipflop.

 

Synchronous counter.

All Flip Flops in these driven by same CLK

For Down

 

- Here all clks are joined to ~~make~~ single CLK and Master resets of 3 flip-flops connected as one MR

- Design : How we shall decide to <sup>give</sup> input J & K to these Flip-flop such that required output is observed.



Now How  $J_2, K_2, J_1, K_1, J_0, K_0$  is given to give output as given  $Q_2, Q_1, Q_0$ .

- In every next state output  $Q_0$  is always toggles. Hence for toggle  $J_0=1$  &  $K_0=1$

Now,

- Next state of  $Q_1$  depend on  $Q_0$  (current state)

IF  $Q_0$  is 0 then next state of  $Q_1$  is continuous

IF  $Q_0$  is 1 then  $Q_1$  is toggle (change)

$Q_0$  direct connect to  $J_1, K_1$  (output) (Common input of FF1)

Hence,  $J_1, K_1$   
 $Q_0, Q_0$

IF  $Q_0=0$  then  $Q_1=0$

$Q_0=1$  continue  $Q_1=0$

$Q_0=0$  toggle  $Q_1=1$

- Deciding for FF 2 see output of  $Q_1$  &  $Q_0$

FF-2 toggles when output of  $Q_1$  &  $Q_0$  both 1

- Put AND Gate betn  $Q_1, Q_0$  &  $J_2, K_2$  we can.

$J_2, K_2$		$Q_1, Q_0$		$Q_1, Q_0$	
$J_2$	$K_2$	$Q_1$	$Q_0$	$Q_1$	$Q_0$
1	1	$Q_1$	$Q_0$	$Q_1$	$Q_0$

### \* 3 Bit - [DOWN COUNTER]

What input.

$J_0$	$K_0$	$J_1, K_1$	$J_2$	$K_2$	$Q_2$	$Q_1$	$Q_0$
1	1	$\bar{Q}_1, \bar{Q}_0$	$\bar{Q}_1, \bar{Q}_0$	$\bar{Q}_1, \bar{Q}_0$	1	1	1
					1	0	1
					0	1	1
					0	0	1
					0	0	0
					1	0	0
					1	1	0
					1	1	1

AS Reverse UP-counter Conditions.

IF  $Q_0$  is 0 then next state of  $Q_1$  is toggle.  
IF  $Q_1, Q_0$  is 0 then toggling for  $Q_2$ .




☐ ☐ ☐


PAGE NO.

Decade counter  $\leftarrow$  (has 10 states)

Using 4 bits 16 states possible but not use of all uses only 10 states
 
$$T_b k_0 \otimes \mathbb{Q}, \mathbb{Q}_0$$


- next output state as expected.

 

if  $Q_1$  is 0 then  $Q_0$  toggle  
if  $Q_1$  is 1 in  $Q_0$  continue.

\* Decode Counter [10 state]



$T_0, K_0$	$J_1, K_1$	$J_2, K_2$	$J_3, K_3$	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	$Q_0(\overline{Q_3} \overline{Q_2} \overline{Q_1})$	$Q_1 \overline{Q_0}$	$Q_2 \overline{Q_1} \overline{Q_0}$	0	0	0	0
1				0	0	0	1
2				0	0	1	0
3				0	0	1	1
4				0	1	0	0
5				0	1	0	1
6				0	1	1	0
7				0	1	1	1
8				1	0	0	0
9				1	0	0	1
10				1	0	1	0

$J_1, K_1 = Q_0$   $Q_3 Q_2 Q_1$  should not be 1 0 0  $\Rightarrow$


$J_1, K_1 = 0$  when either  $Q_0 = 0$  or  $Q_3 Q_2 Q_1 = 100$

$J_1, K_1 = Q_0 \cdot (\overline{Q_3} \overline{Q_2} \overline{Q_1})$  is 0 when  $(Q_3 Q_2 Q_1 = 100)$

$$J_3, K_3 = Q_2 Q_1 Q_0 + Q_3 \cdot Q_0$$

$$= Q_0 (Q_2 Q_1 + Q_3)$$

\* Asynchronous counter.

 

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1