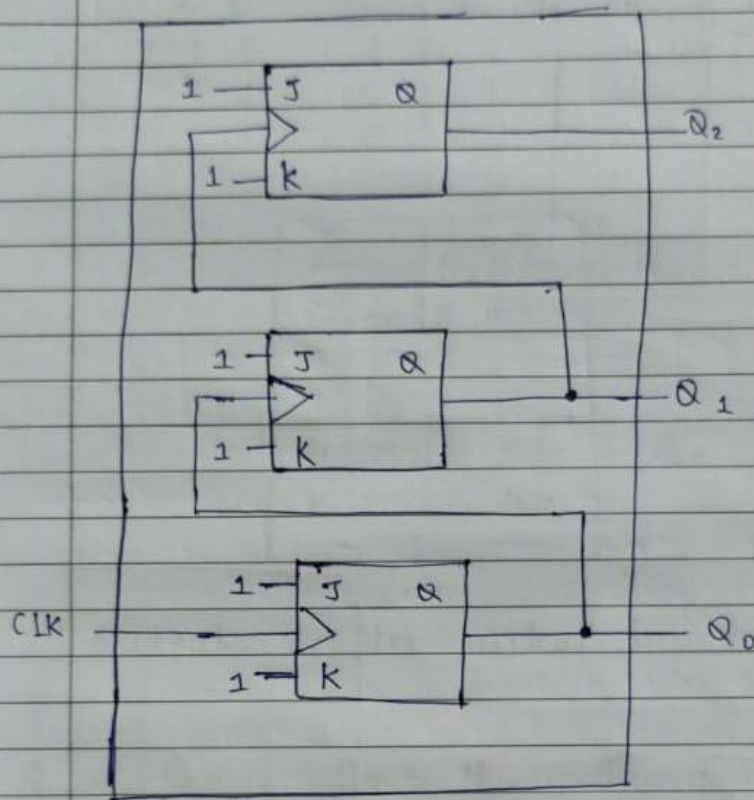


Name - Khushi Nitinkumar Patel.
PRN - 2020BTECS00037.
Branch - CSE.


- Asynchronous counter -

Clock is given only to the least significant flip flop, in an asynchronous counter.




Q ₂	Q ₁	Q ₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

• Shift Registers :-

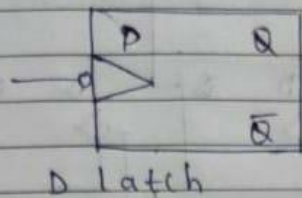


Truth table :-

clk	Q
0, 1, ↑	Last state
↓	D

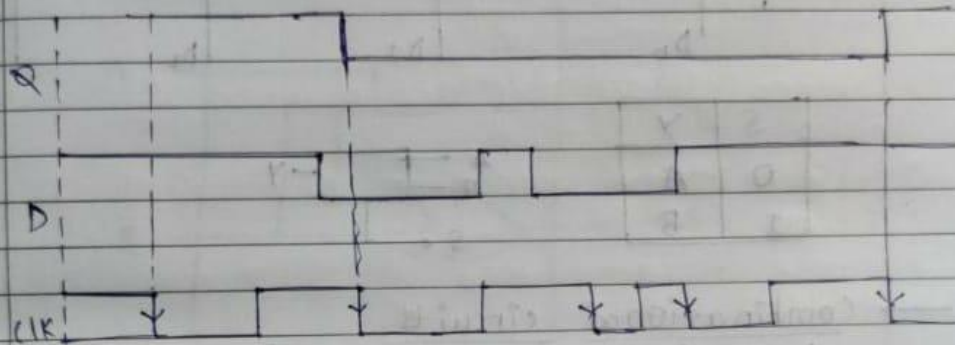


• 4 bit shift register.

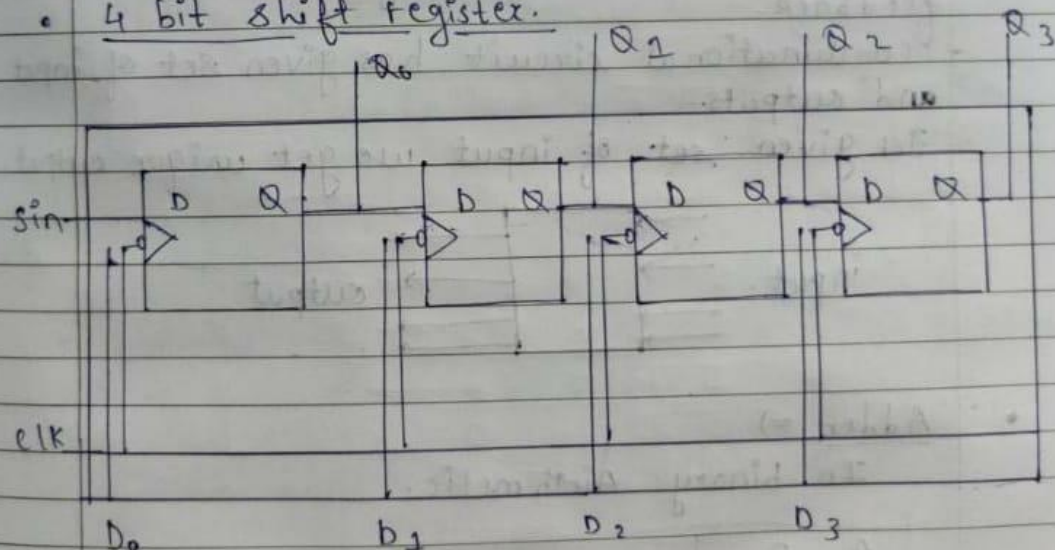


sin = 0

Q3	Q2	Q1	Q0
1	0	1	1
0	1	1	0

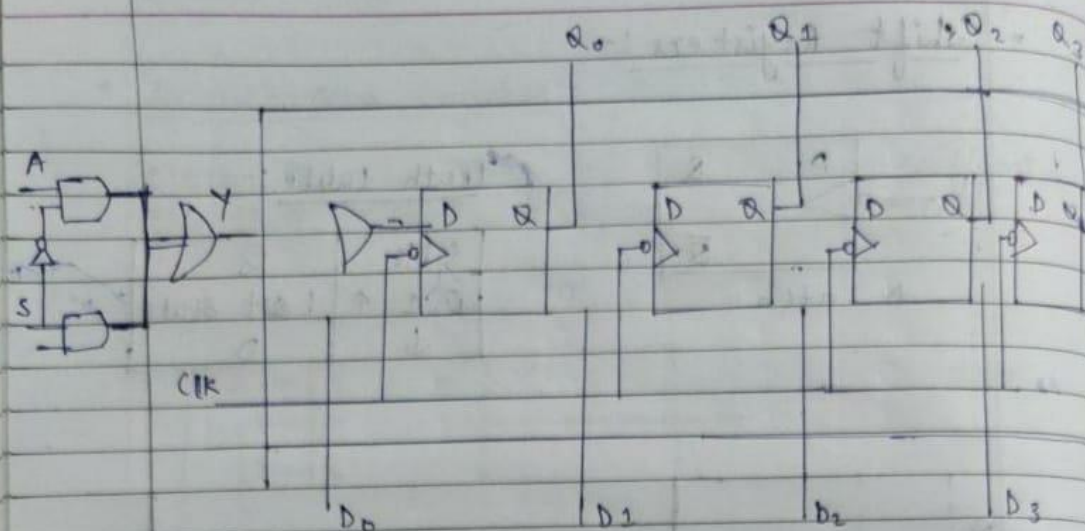

S	Y
0	A
1	B

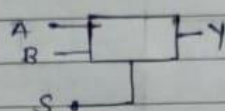

→ Combinational circuits.


- It consists of interconnection of gates to each other and cascading them with no feedback.
- Combinational circuit has given set of input and outputs.
- For given set of input, we get unique output.



• Adder ⇒

In binary Arithmetic.

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

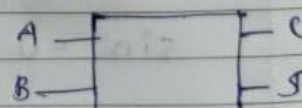


Adding 2, 1 bit number

Explanation:

0	0	1	1
+ 0	+ 1	+ 0	+ 1
0 0	0 1	0 1	1 0
↑ ↑			
c	s		

If both A & B are 1 then carry = 1

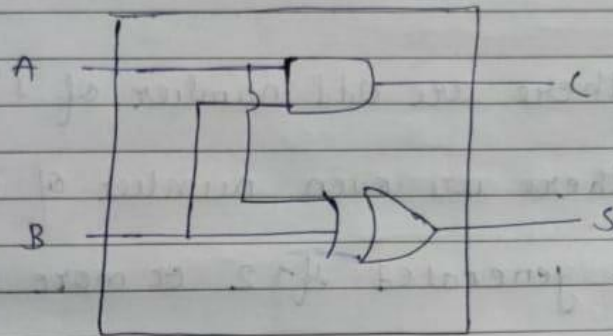


Half Adder.

- Adding 2, 2 bits number.

e.g

	A_1	A_0
	B_1	B_0
C_1	C_0	
C_1	S_1	S_0

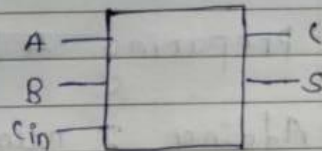

- Addition of 2 bit number is 3 bit number
- Here we need full adder.

Truth table of full adder =>

Cin	A	B	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


- 1) when there are odd number of 1's, sum is 1.
- 2) when there are even number of 1's, sum is 0.
- 3) carry is generated if 2 or more 1's are there.

- 2 half adder and 1 OR gate is used to prepare full adder.

• Preparing 4 bit full adder :-

Adding 2 numbers of 4 bits.

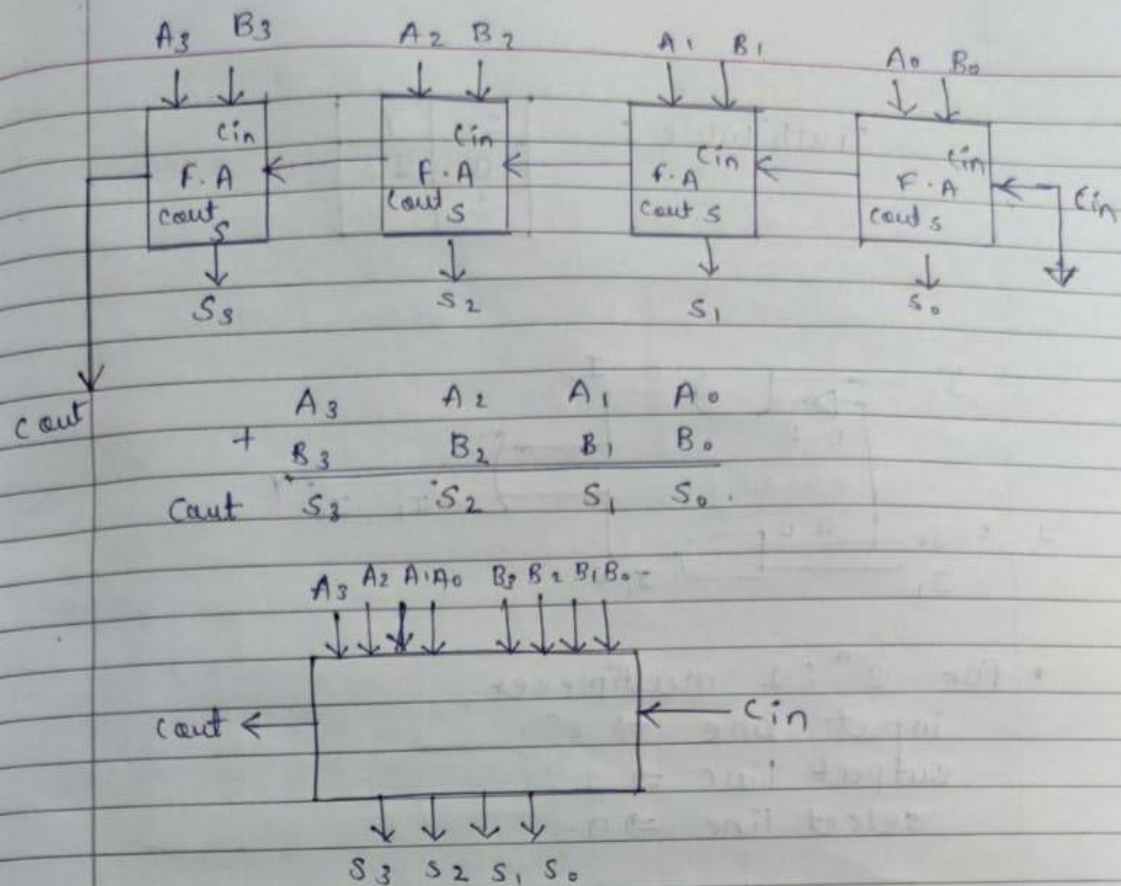
$$\begin{array}{r}
 \text{c.g.} \quad 0 \ 1 \ 0 \ 1 \ \leftarrow A \\
 \quad \quad 1 \ 1 \ 0 \ 1 \ \leftarrow B \\
 \quad \quad \underline{1 \ 1 \ 0 \ 1 \text{ Cin}} \\
 \quad \quad 1 \ 0 \ 0 \ 1 \ 0
 \end{array}$$



A 4 bit full adder comprises of 1 carry in, 1 carry out, 2, 4 bit inputs A and B, 1, 4 bit output sum.

→ Multiplexer. \Rightarrow (many as to 1).

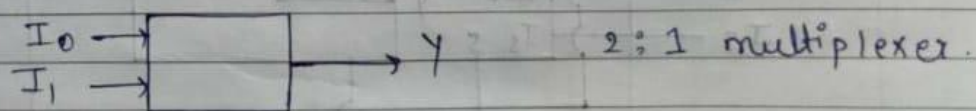
- A multiplexer consists of more than 1 inputs and only single output.



- S_0 is select line the decides which input should come on the output.


Truth table :-

s_0	Y
0	I_0
1	I_1

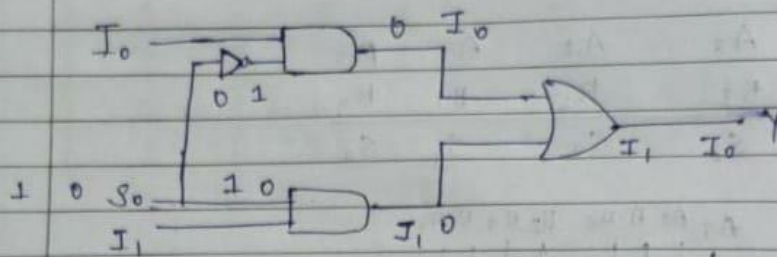

- for $2^n : 1$ multiplexer,
input line $\Rightarrow 2^n$.
output line $\Rightarrow 1$.
select line $\Rightarrow n$.

• 4:1 multiplexer

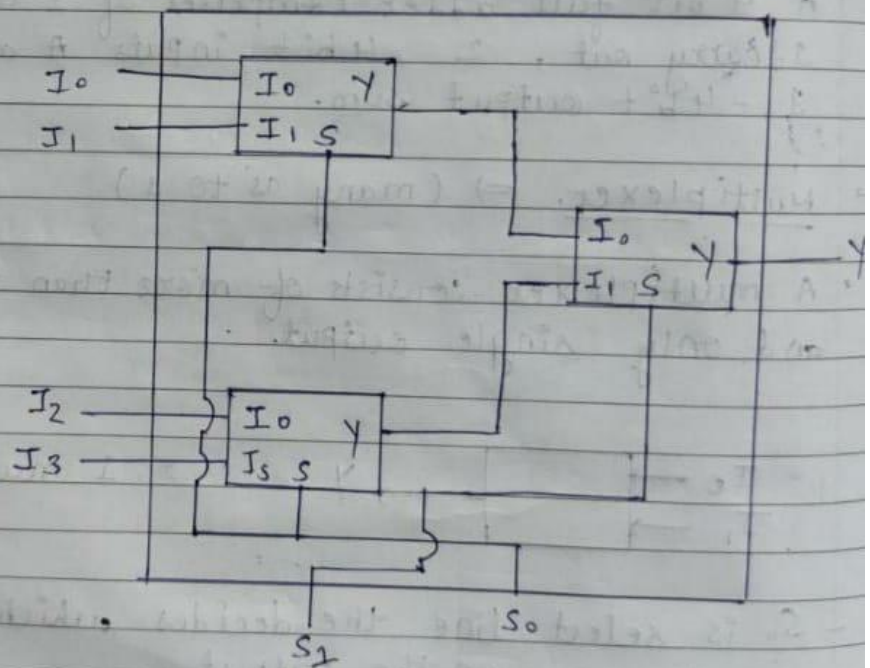

1) $S_1 = 0$, Top multiplexer O/P appears on final O/P.

2) $S_1 = 1$, Bottom multiplexer O/P appears on final O/P.


Truth table :-

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

- S_0 decides which output should appear on 1st layer multiplexer.
- S_1 decides final O/P.

• Arduino board ⇒

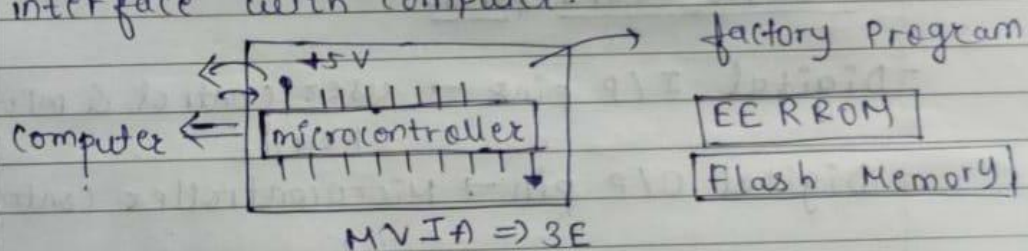- It consists of microcontroller chip, it is having interface with computer.



Microcontroller = Microprocessor + memory + I/O devices.


- Microcontroller chip consists of supply pins and I/O pins

- Microcontroller chip consist of supply pins and I/O pins.

- Power on reset circuit \Rightarrow Reset the circuit and Microprocessor starts program from Address 0, which is present in memory.

Factory programmed.

EEPROM
Flash memory.

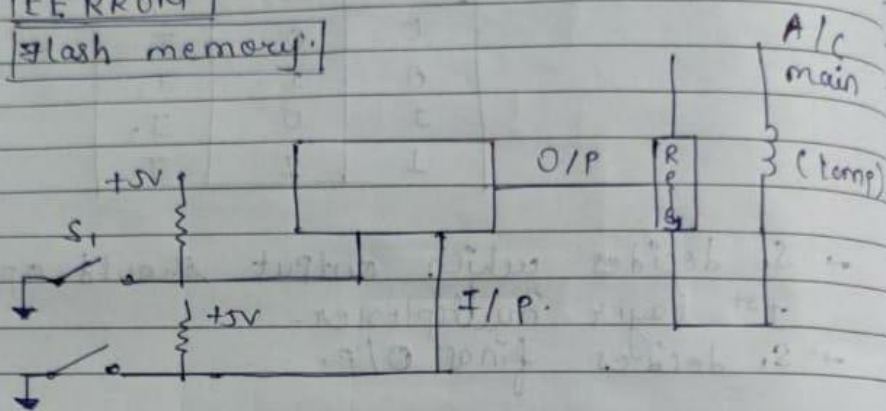


$$y = S_1 \oplus S_2$$

\rightarrow Arduino board pins.

- Digital I/P pins \rightarrow user control & microcontroller read.


- Digital O/P pin \rightarrow Microcontroller controls it.

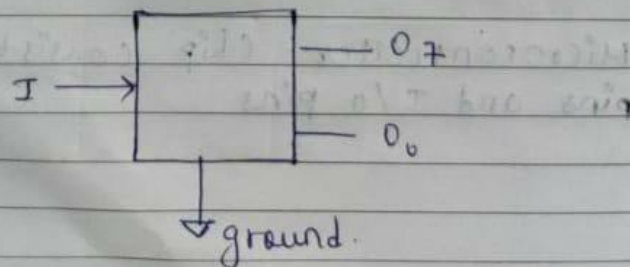- Analog to Digital ~~controller~~ converter (ADC).




Input in range of 0 to 5V is converted into output 00-FF (80H)
 $\frac{5}{255} \Rightarrow 1 \text{ UNIT.}$

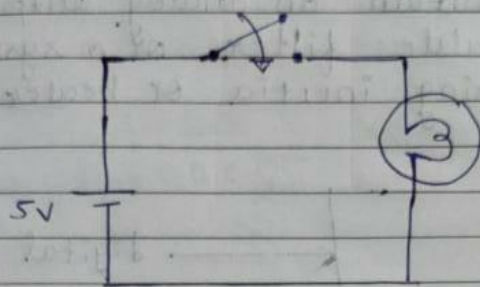
- Analog O/P pin is not available, but output is generated in another form i.e. pulse width modulated form (PWM).




- To change intensity of lamp with no resistor and constant voltage supply.
- If ON/OFF takes place at rapid rate, then filament will be heated at average rate.
- Pulse width modulation O/P generates a square wave where duty cycle can be from 0% to 100%.

Square wave \Rightarrow

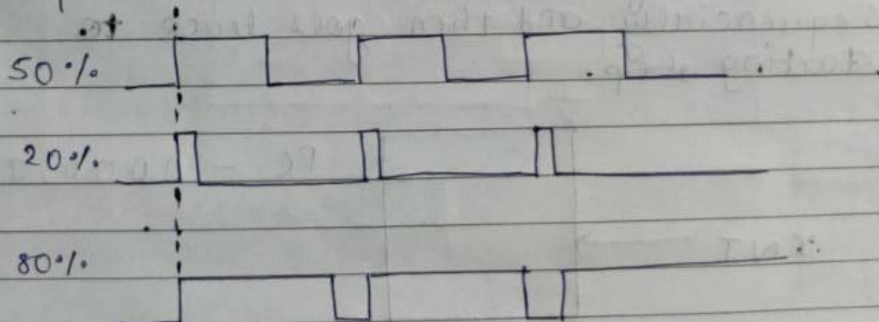

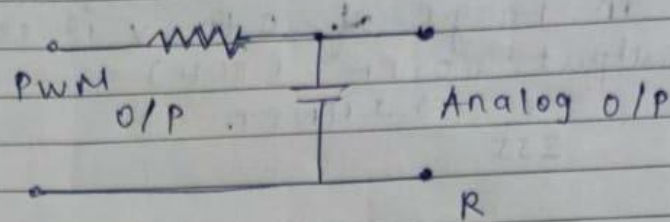

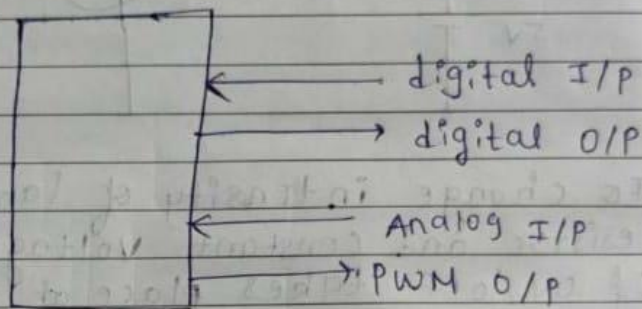
- PWM output pin is a digital output pin in which by controlling its duty cycle it is possible to obtain an analog output by putting suitable filter or a system which itself is having inertia or heater.





Arduino board

• Interrupt Inputs

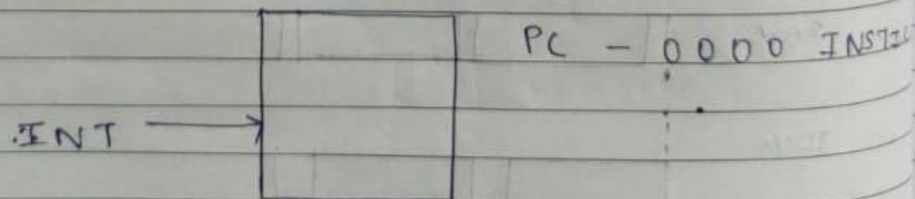- A program on arduino board consist of sequence of instruction, which are executed sequentially and then goes back to starting step.



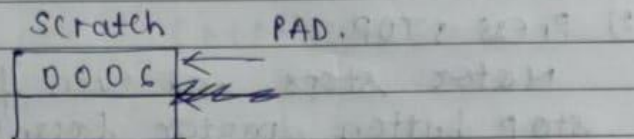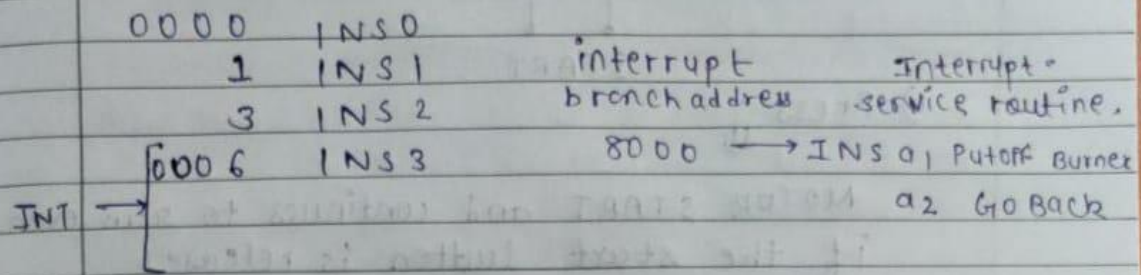- Interrupt is an input pin which is checked after instruction, automatically.
- It doesn't consume any time.



• Arduino programming.

General purpose Digital I/O pins

I/P pin → switch → Manual switch

O/P pin → Read P0.0

Input P1.1


- output pin will be made to logic '1' or logic '0' by microcontroller.


SET P1.2

RESET P2.1

WRITE (P1.3, FLAG)

OUTPUT (P3.2, 0).

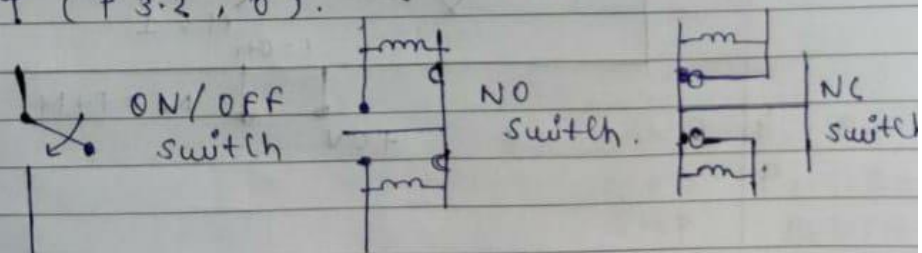

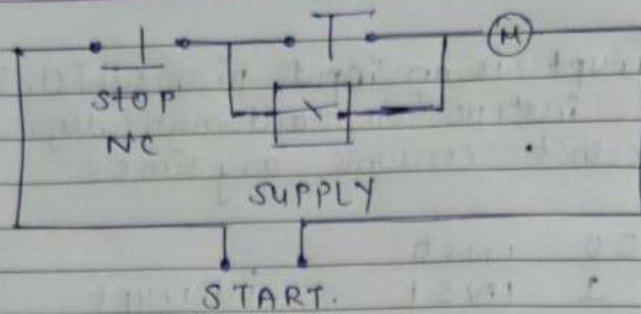



1) Press



MOTOR START and continues to run even if the start button is released

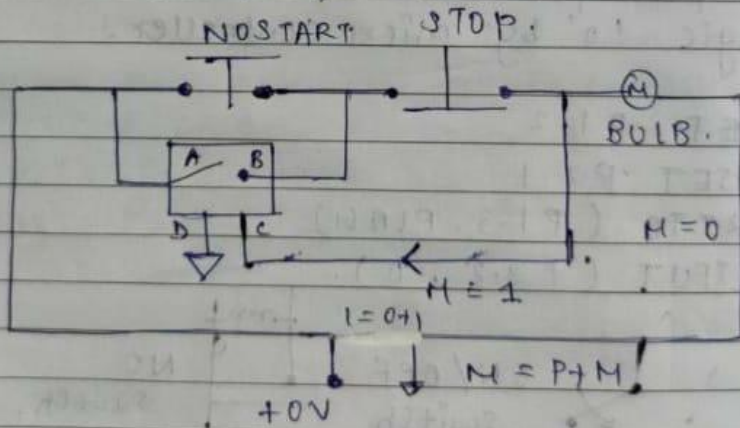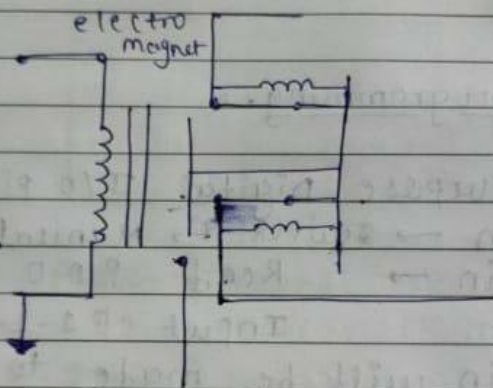2) Press STOP

Motor stops and even if you release stop button, motor doesn't stop.



When start button is pushed, motor starts, bulb glows and relay.

Using start button, motor can be started and using stop button motor can be stopped.

READ START

READ STOP


$M = (P + M) \cdot \bar{Q}$

label $P = \text{INPUT}(\text{START})$

$Q = \text{INPUT}(\text{STOP})$

$M = (P + M) \cdot \bar{Q}$

STOP	START	M
1	X	OFF(0)
0	1	ON(1)
0	0	0/1

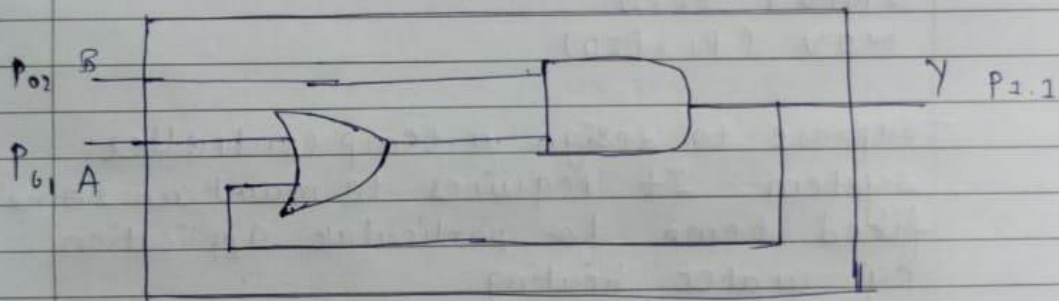

$$Y = C \cdot B$$

$$Y = (A + Y) \cdot B$$

$\begin{matrix} B_0 & B_1 & B_2 \\ \uparrow & \uparrow & \uparrow \\ A & B & Y \end{matrix} \Rightarrow \text{internal registers.}$

$B0 = \text{READ } P0.1$

BEGIN : MOV B0, P0.1 AND B2, B1
 MOV B1, P0.2 MOV P11, B2
 OR B0, B2 IMP BEGIN

Microcontroller instructions are either arithmetic logic instruction or input/output instructions.

• Analog I/P, PWM O/P.

Analog I/P is there are inbuilt analog to digital converters and it is possible to read that pin.

5V	→ 2550	3 Bits	Analog
S1	→ 255	P2.0	0 0
		P2.1	1
5000 mV = 20 mV		P2.3	1
250			1
			1
		P2.7	FF

INPUT P2.0

MOV (R1, P20)

- Suppose to design a temp controller system. It requires to maintain some fixed temp for particular application. eg water heating.



Maintain
fixed temp
which should be
pre-attable

8 switches

00 - FF

PWM

100 sec

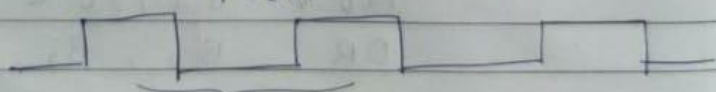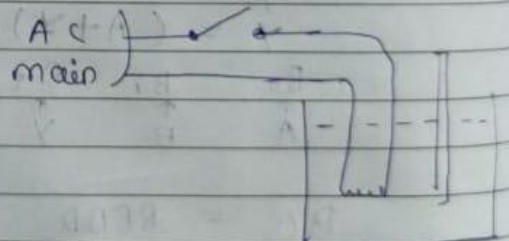

(S.P)

user sets set point \rightarrow Read by Arduino
System process (P.V) \rightarrow Read by Arduino
changes variables.

SWITCH

O/P Pin \leftarrow controlled by Arduino.
(READ)